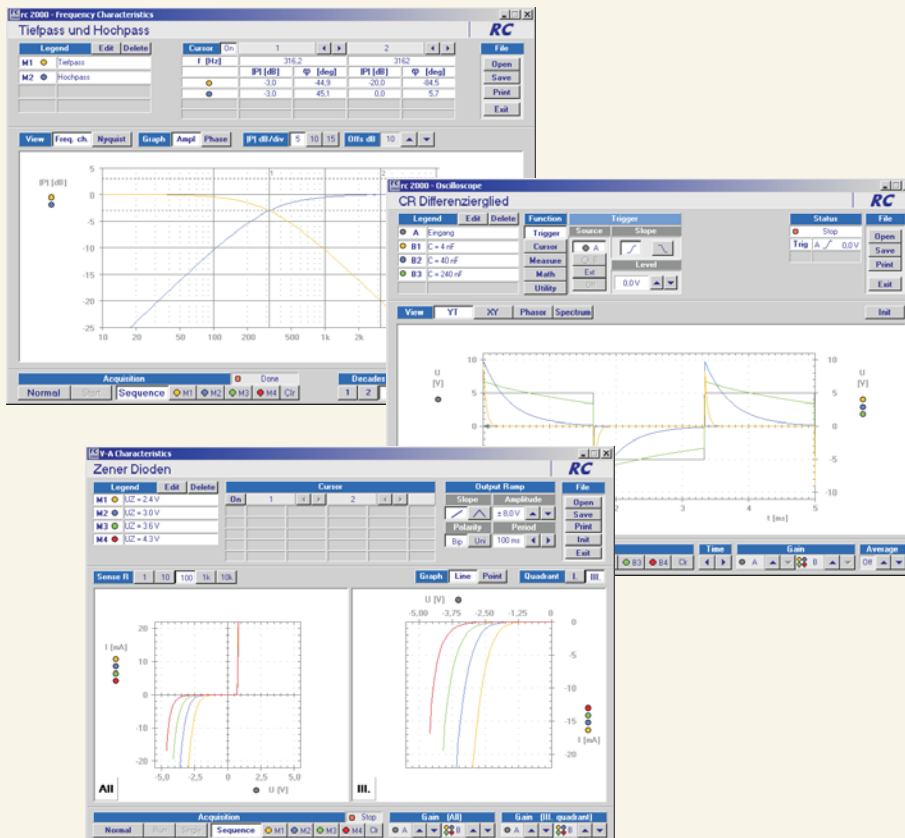


# System rc2000 - $\mu$ LAB

## Inspiration





## Contents

### **AC Circuits**

RC Integrator and CR Differentiator	3
Low- and High-Pass Filter - Time Domain	4
Low- and High-Pass Filter - Frequency Domain	5
Series RLC Resonant Circuit	6
Series RLC Band-Stop Filter	7
Series RLC Band-Pass Filter	8
T - Network	9

### **Electronic Devices**

Linear Resistors	10
Si Diodes	11
LED Diodes	12
Zener Diodes	13
Diode Limiter	14

### **OP-AMP Circuits**

Comparator with Hysteresis	15
Differential Amplifier	16
Astable Multivibrator	17
Phase-Shift Circuit	18

### **Rectifiers**

Half-Wave Rectifier	19
Full-Wave Rectifier	20
Half-Wave Precision Rectifier	21





# RC Integrator and CR Differentiator

## Exercise

Square waves are applied to the input of the RC circuit (integrator) and the CR circuit (differentiator). Display the output of both circuits at different settings of the time constant.


## Schematics

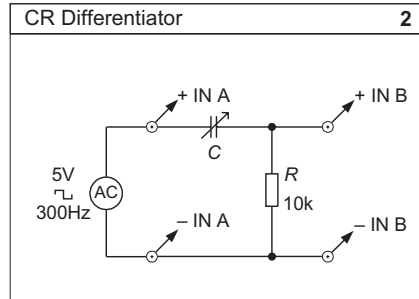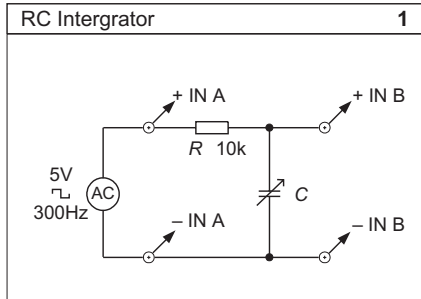

Time constant:


$$\tau = R \cdot C$$

## Result

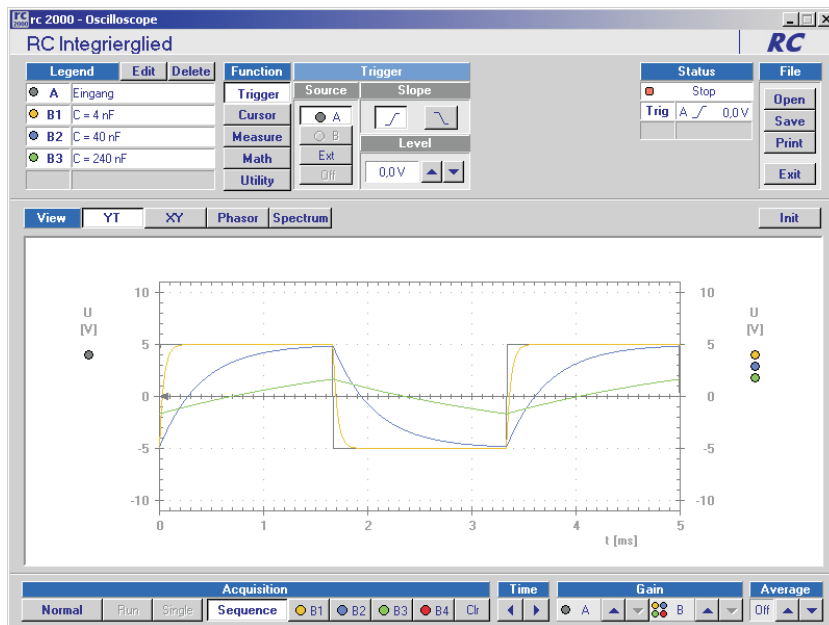
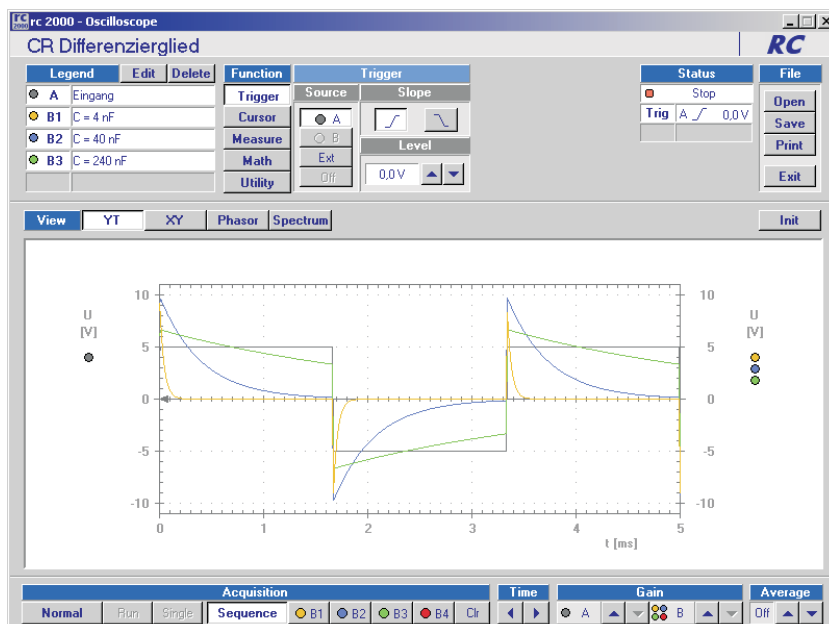
### Integrator - Time constant

- $\tau = 0,04 \text{ ms}$  ( $C = 4 \text{ nF}$ )
  - $\tau = 0,4 \text{ ms}$  ( $C = 40 \text{ nF}$ )
  - $\tau = 2,4 \text{ ms}$  ( $C = 240 \text{ nF}$ )
- Integration



### Differentiator - Time constant:



- $\tau = 0,04 \text{ ms}$  ( $C = 4 \text{ nF}$ )
  - $\tau = 0,4 \text{ ms}$  ( $C = 40 \text{ nF}$ )
  - $\tau = 2,4 \text{ ms}$  ( $C = 240 \text{ nF}$ )
- Differentiation

# Low- and High-Pass Filter - Time Domain

## Exercise

Display the voltage curves and phasors of the low-pass and high-pass filter at an equal cutoff frequency.

## Schematics

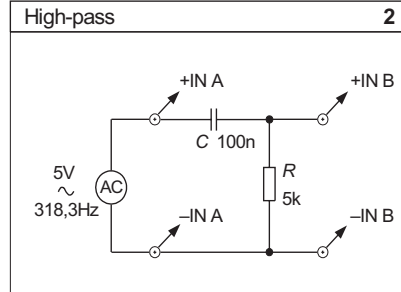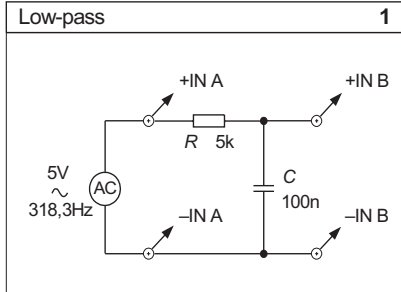


Cutoff frequency (-3dB):

$$f_G = \frac{1}{2\pi RC}$$

Phase shift:

$$\varphi = \pm 45^\circ$$


## Result

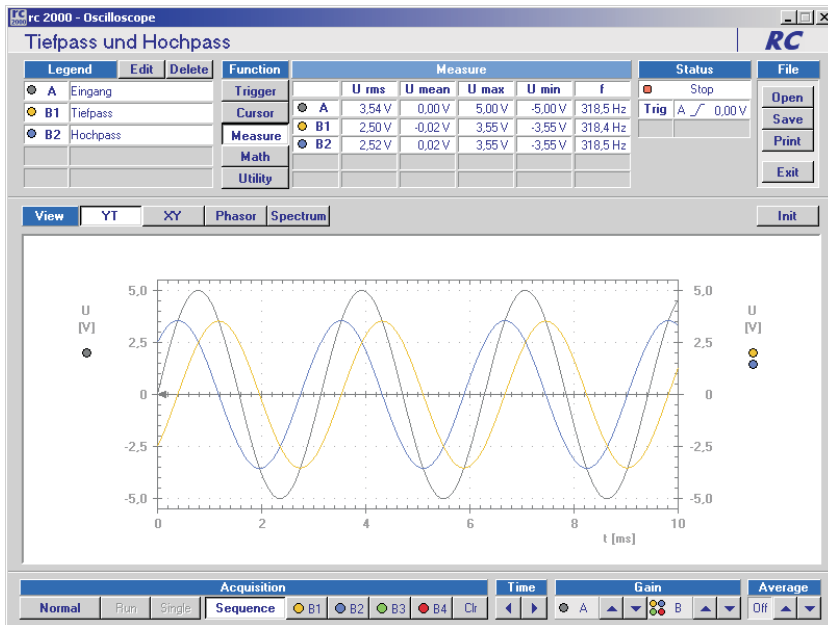

### Time curves:

- Low-pass
- High-pass

$$f_G = 318,3 \text{ Hz}$$

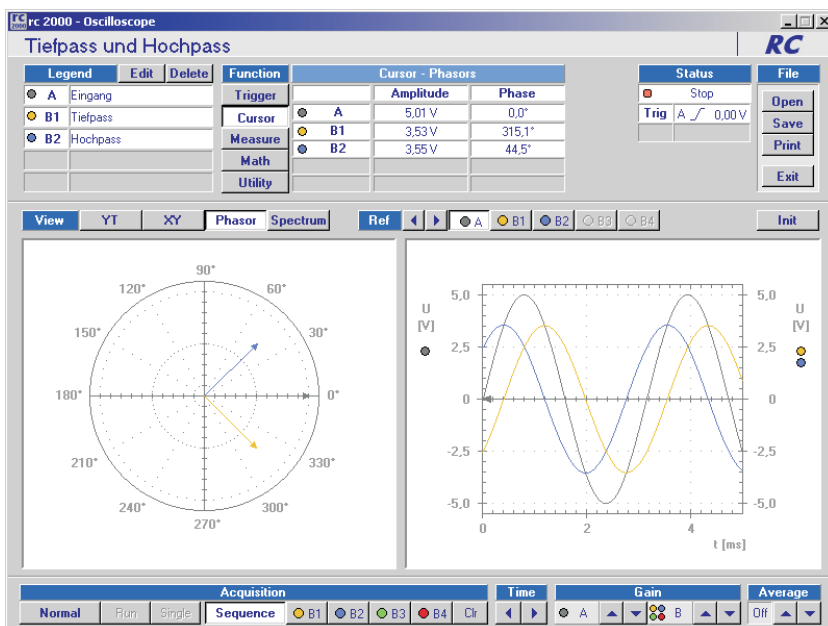

### Phasor and time diagram:

- Low-pass
- High-pass



$$f_G = 318,3 \text{ Hz}$$

# Low- and High-Pass Filter - Frequency Domain

## Exercise

Measure the amplitude and phase frequency characteristics at an equal cutoff frequency.

## Schematics

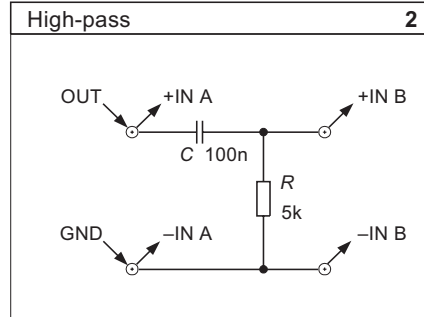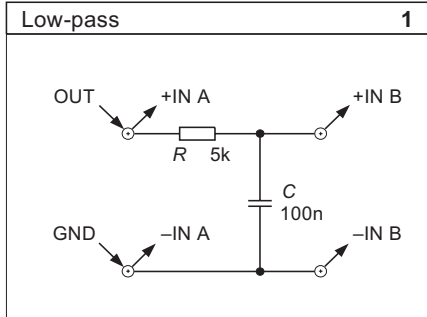


Cutoff frequency (-3dB):

$$f_G = \frac{1}{2\pi RC}$$

Phase shift:


$$\varphi = \pm 45^\circ$$

## Result

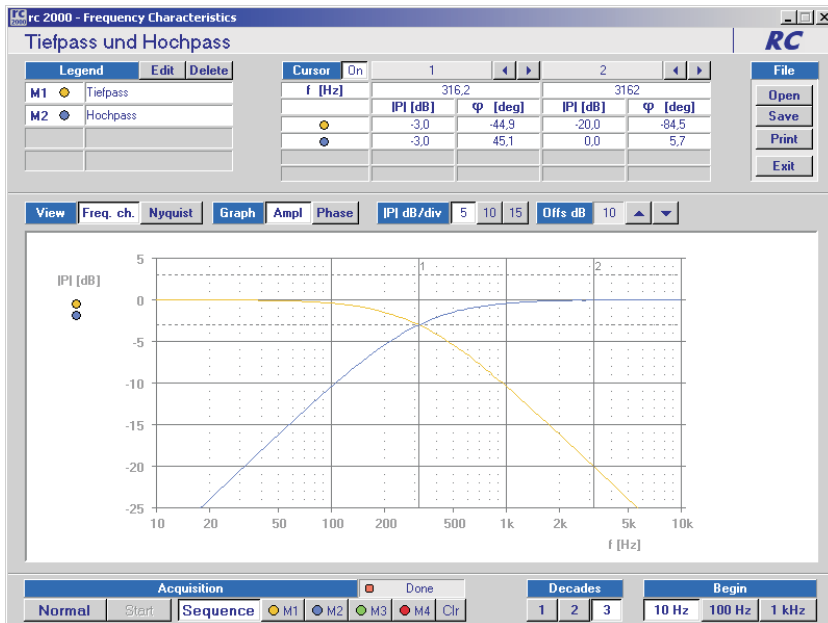
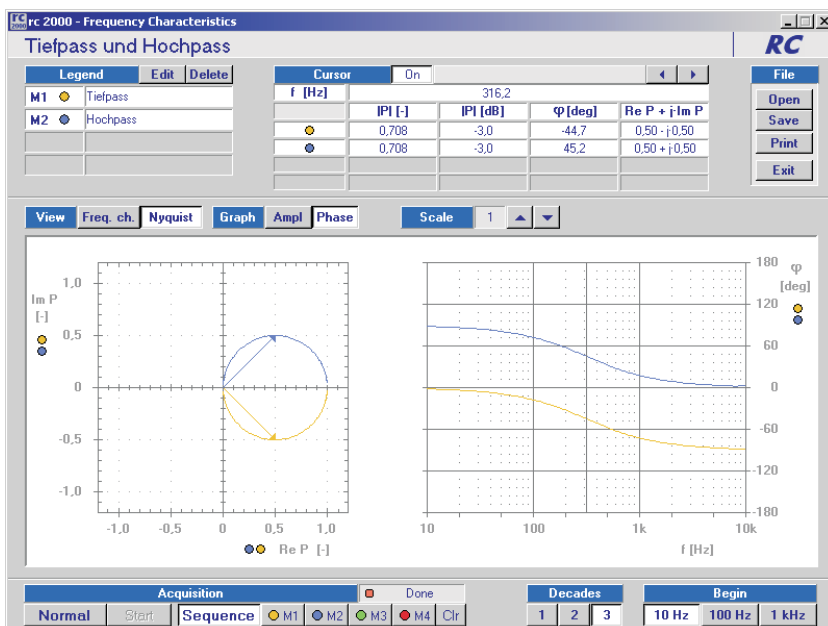
### Amplitude characteristics:

- Low-pass
  - High-pass
- $f_G = 318,3 \text{ Hz}$



### Nyquist + Freq. characteristics:

- Low-pass
  - High-pass
- $f_G = 318,3 \text{ Hz}$



# Series RLC Resonant Circuit

## Exercise

Display the voltage curves across the R,L,C of the series circuit for two cases:

- 1) C - ideal, L - ideal
- 2) C - ideal, L - real


## Schematics

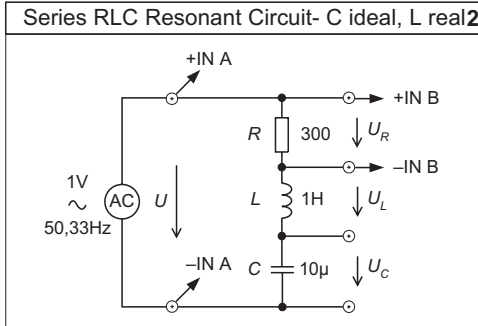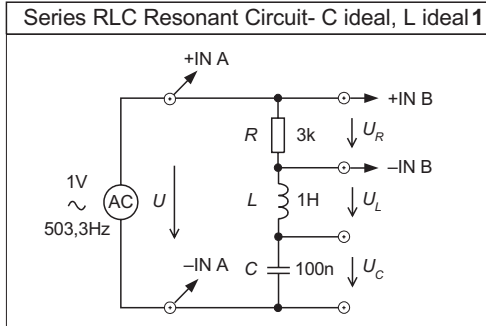

Resonant frequency:

$$f_R = \frac{1}{2\pi\sqrt{LC}}$$


## Result

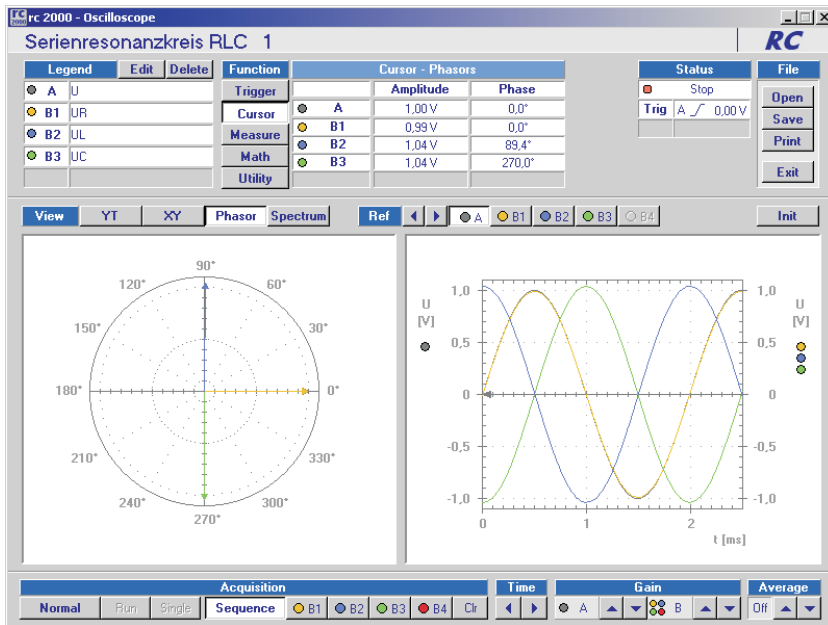
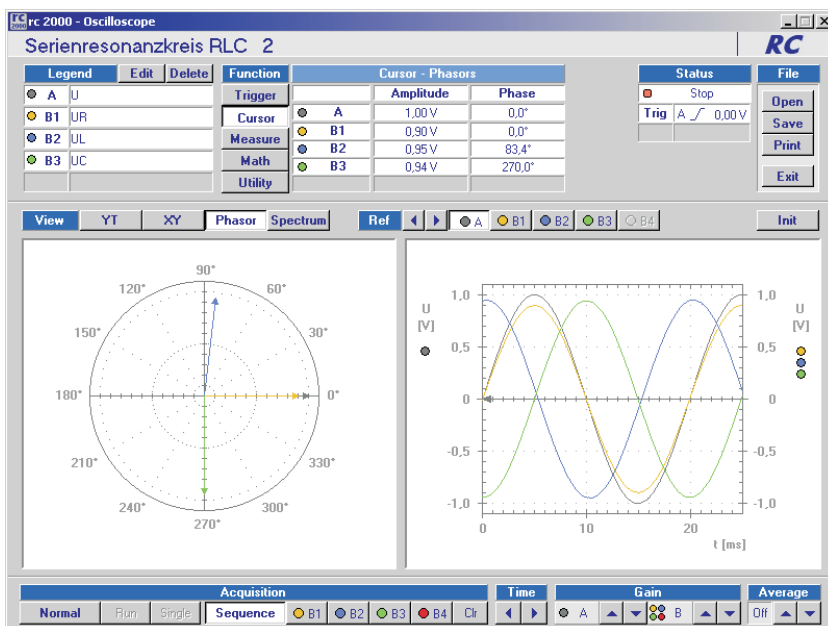
### Circuit 1 - C ideal, L ideal:

- U<sub>R</sub>
- U<sub>L</sub>
- U<sub>C</sub>

$$f_R = 503,3 \text{ Hz} \quad Q \approx 90$$



### Circuit 2 - C ideal, L real:

- U<sub>R</sub>
- U<sub>L</sub>
- U<sub>C</sub>

$$f_R = 50,33 \text{ Hz} \quad Q \approx 9$$




# Series RLC Band-Stop Filter

## Exercise

Measure the amplitude and phase frequency characteristics of the series band-stop filter at different damping resistors.


## Schematics

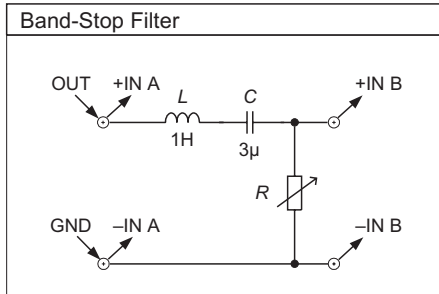

Resonant frequency:

$$f_R = \frac{1}{2\pi\sqrt{LC}}$$


## Result

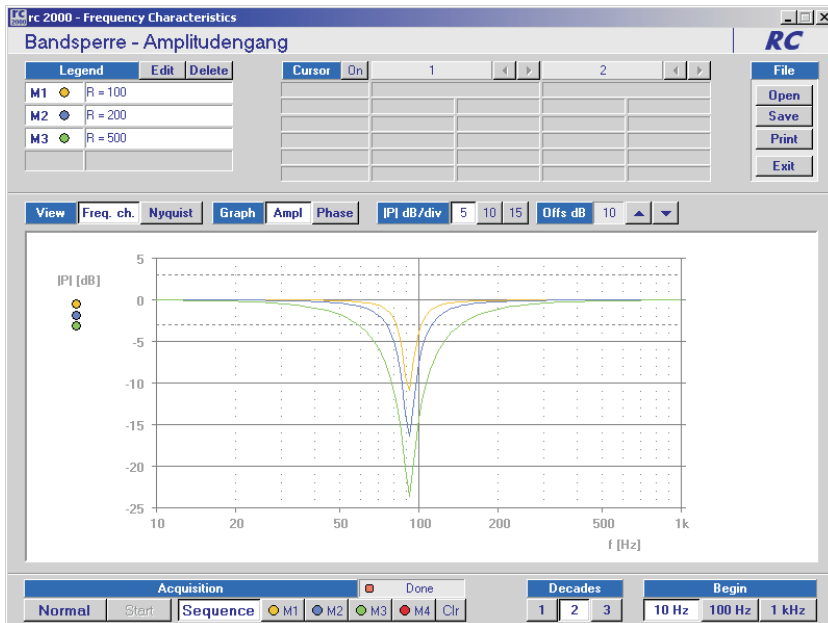

**Amplitude characteristics:**

- $R = 100 \Omega$
- $R = 200 \Omega$
- $R = 500 \Omega$

$$f_R = 91,9 \text{ Hz}$$

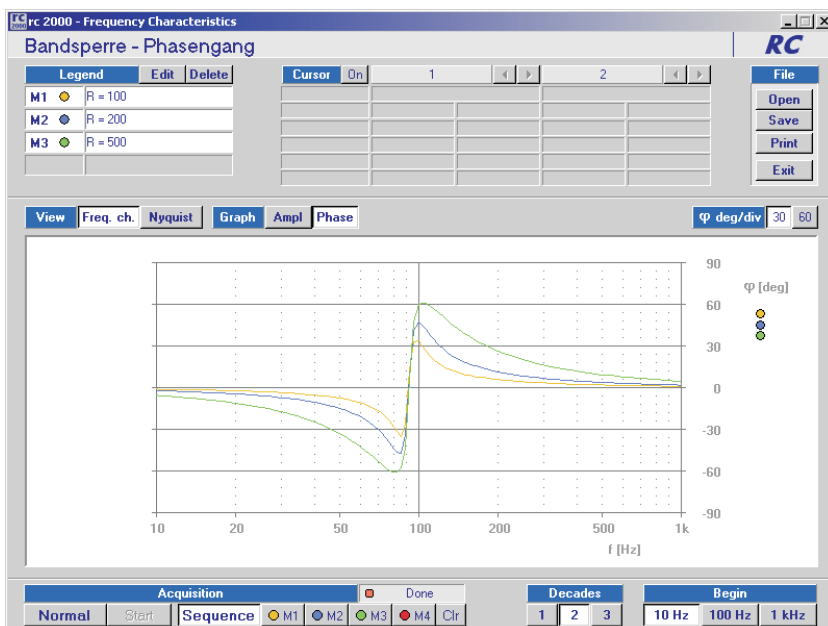

**Phase characteristics:**

- $R = 100 \Omega$
- $R = 200 \Omega$
- $R = 500 \Omega$


$$f_R = 91,9 \text{ Hz}$$

# Series RLC Band-Pass Filter

## Exercise

Measure the amplitude and phase frequency characteristics of the series RLC band-pass filter for different damping resistors.


## Schematics

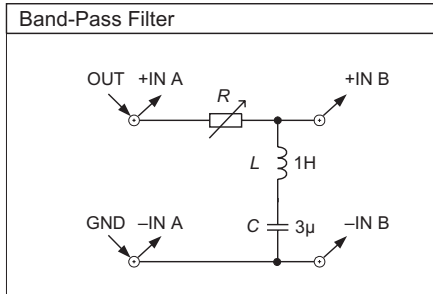

Resonant frequency:

$$f_R = \frac{1}{2\pi\sqrt{LC}}$$


## Result

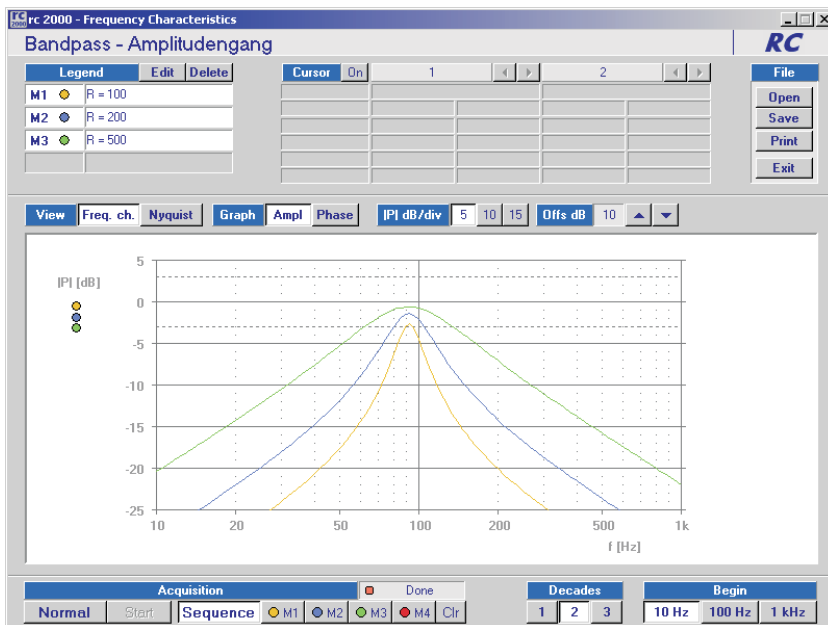

### Amplitude characteristics:

- $R = 100 \Omega$
- $R = 200 \Omega$
- $R = 500 \Omega$

$$f_R = 91,9 \text{ Hz}$$

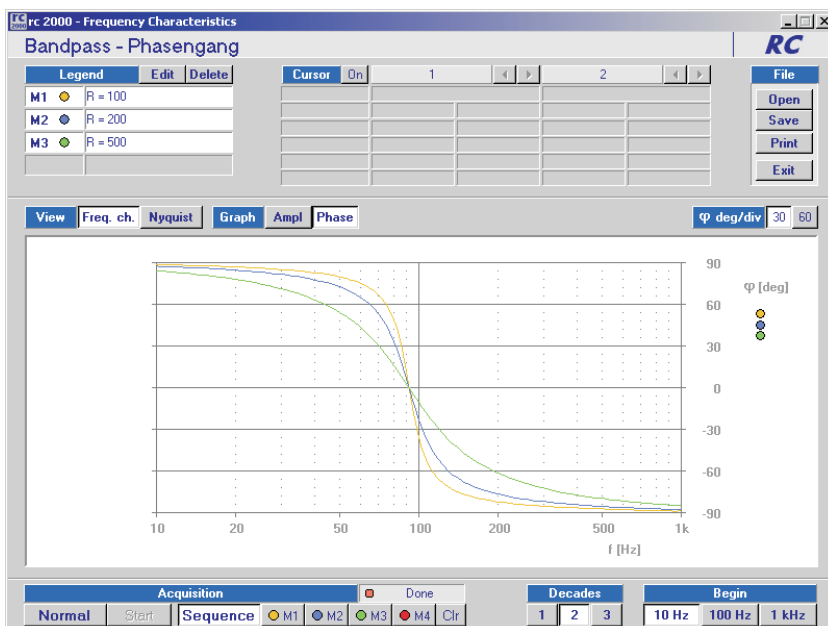

### Phase characteristics:

- $R = 100 \Omega$
- $R = 200 \Omega$
- $R = 500 \Omega$


$$f_R = 91,9 \text{ Hz}$$

# T - Network

## Exercise

Measure the amplitude and phase characteristics of the T-network at different resistor combinations using the equation:

## Schematics

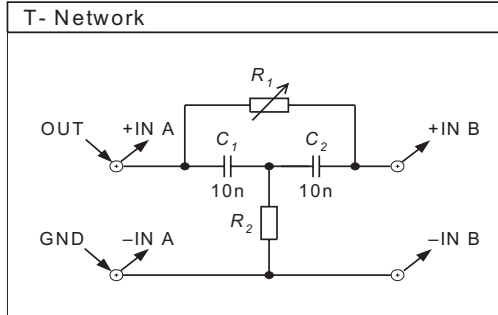


Equation:

$$R_1 \cdot R_2 = konst$$


$$f_R = konst$$

## Result

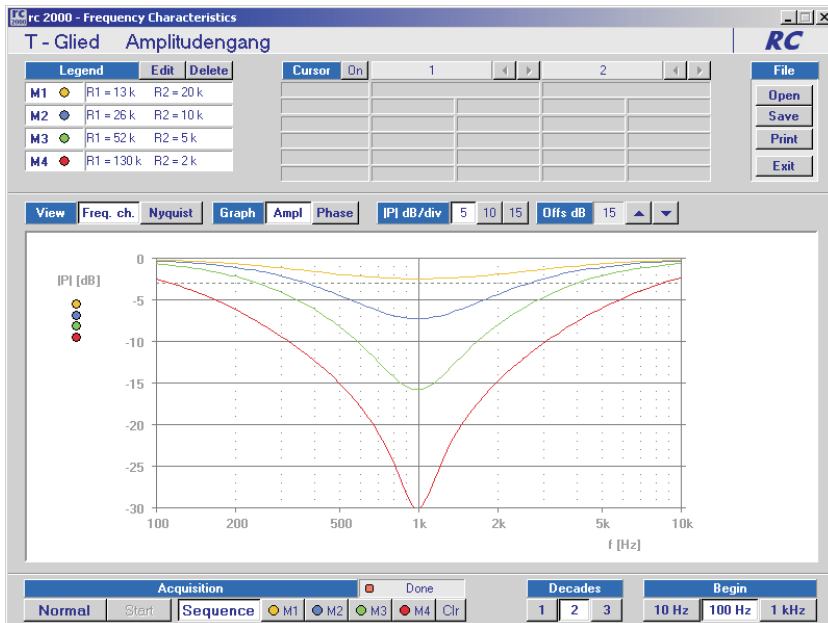
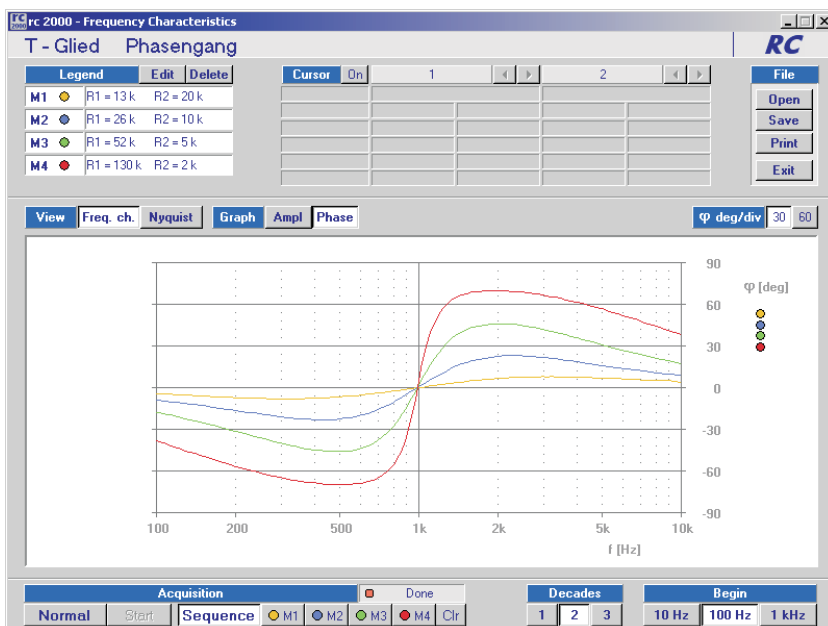
### Amplitude characteristics:

- $R_1 = 13 \text{ k}\Omega$      $R_2 = 20 \text{ k}\Omega$
- $R_1 = 26 \text{ k}\Omega$      $R_2 = 10 \text{ k}\Omega$
- $R_1 = 52 \text{ k}\Omega$      $R_2 = 5 \text{ k}\Omega$
- $R_1 = 130 \text{ k}\Omega$      $R_2 = 2 \text{ k}\Omega$



### Phase characteristics:


- $R_1 = 13 \text{ k}\Omega$      $R_2 = 20 \text{ k}\Omega$
- $R_1 = 26 \text{ k}\Omega$      $R_2 = 10 \text{ k}\Omega$
- $R_1 = 52 \text{ k}\Omega$      $R_2 = 5 \text{ k}\Omega$
- $R_1 = 130 \text{ k}\Omega$      $R_2 = 2 \text{ k}\Omega$

# Linear Resistors


## Exercise

Display the V/A characteristics of different linear resistors.  
Using cursors determine the resistor values.

## Schematics

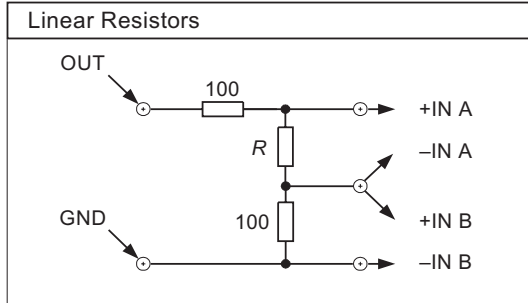

## Result

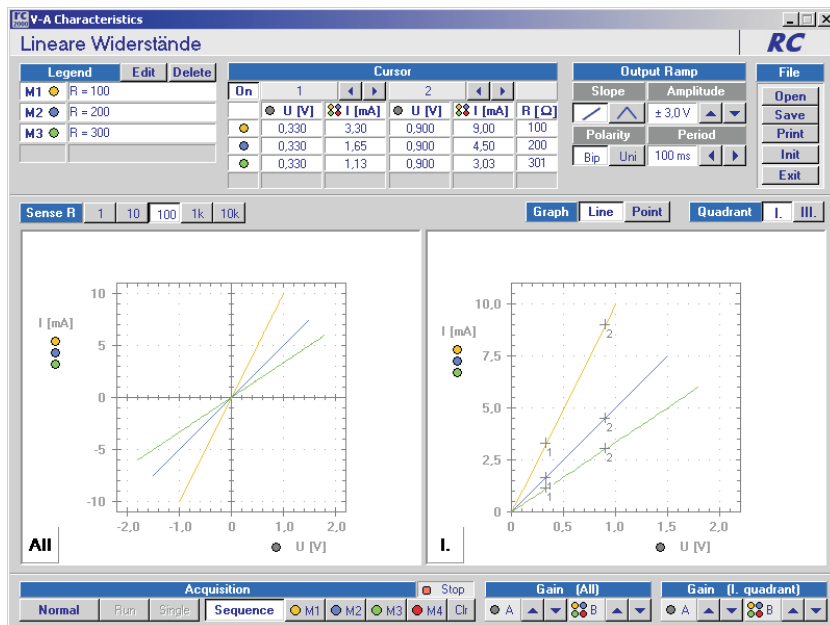

## Linear Resistors:


- $R = 100 \Omega$
- $R = 200 \Omega$
- $R = 300 \Omega$

# Si Diodes


## Exercise

Display the V/A characteristics of two diode types ("normal" and Shottky).

## Schematics

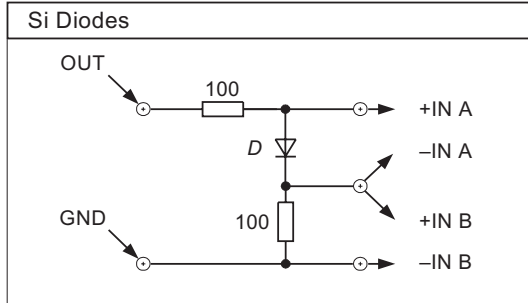

## Result

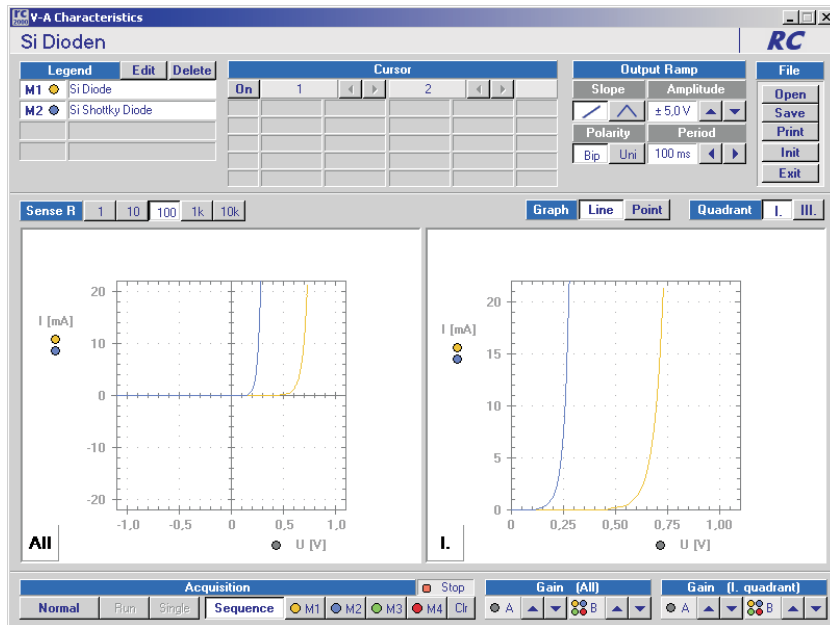

## Si Diodes:


- Si Diode
- Si Shottky Diode

# LED Diodes


## Exercise

Measure the V/A characteristics of the LED diodes ( yellow, blue, green, red).

## Schematics

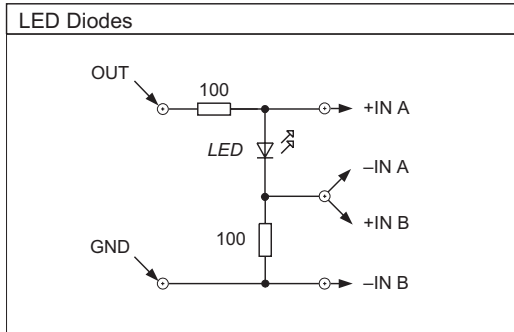

## Result

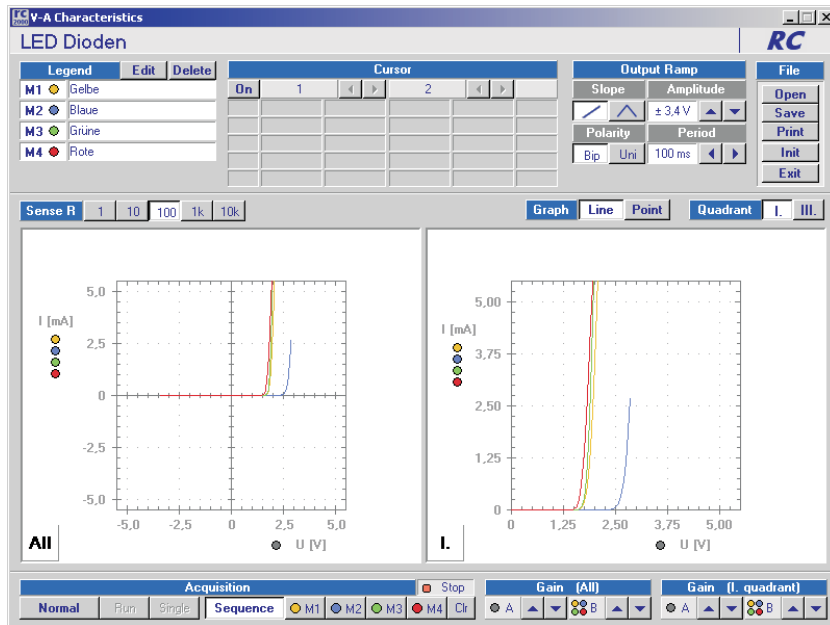

## LED Diodes:


- yellow LED
- blue LED
- green LED
- red LED

# Zener Diodes


## Exercise

Measure the V/A characteristics of the Zener diodes with different Zener voltage  $U_z$ .

## Schematics

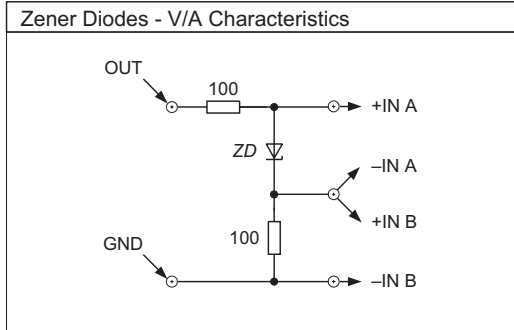

## Result

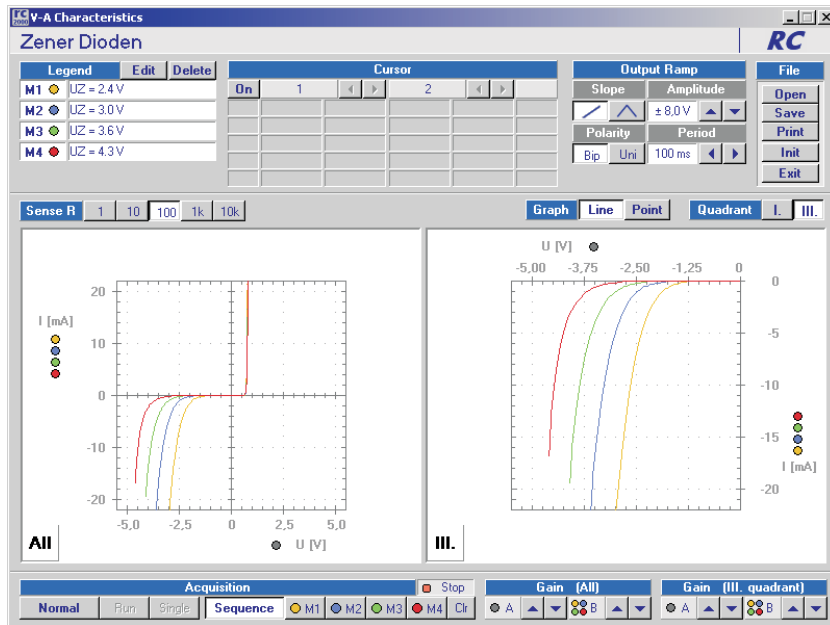

## Zener Diodes:

- $U_z = 2.4 \text{ V}$
- $U_z = 3 \text{ V}$
- $U_z = 3.6 \text{ V}$
- $U_z = 4.3 \text{ V}$

# Diode Limiter



## Exercise

Display the input and output voltage curves of the half-wave diode limiter.


Circuit 1 - limiter without DC

Circuit 2 - limiter with DC

## Schematics

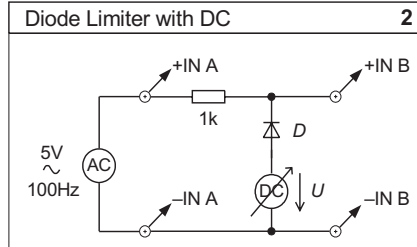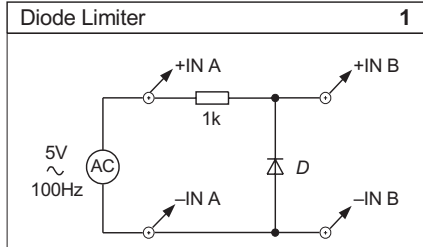


## Result

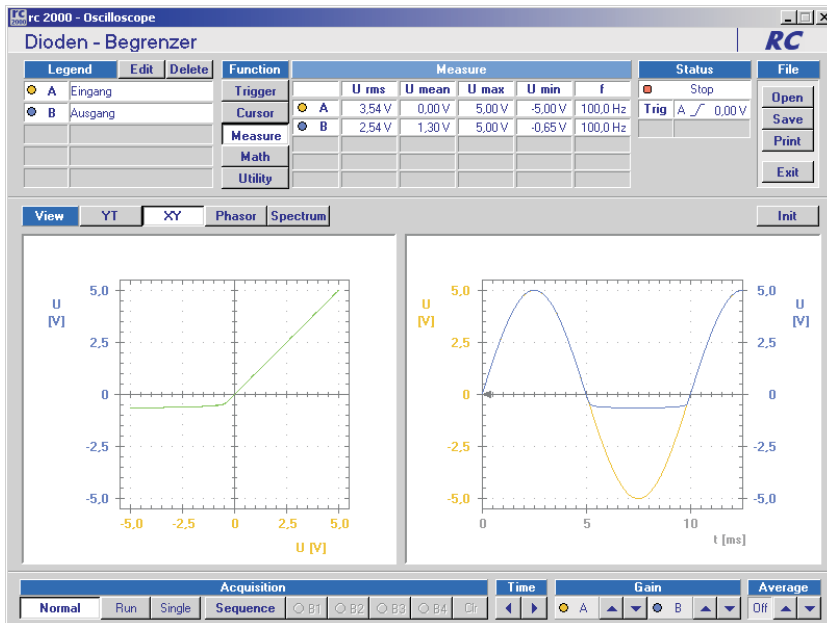

Diode limiter:

- Input
- Output

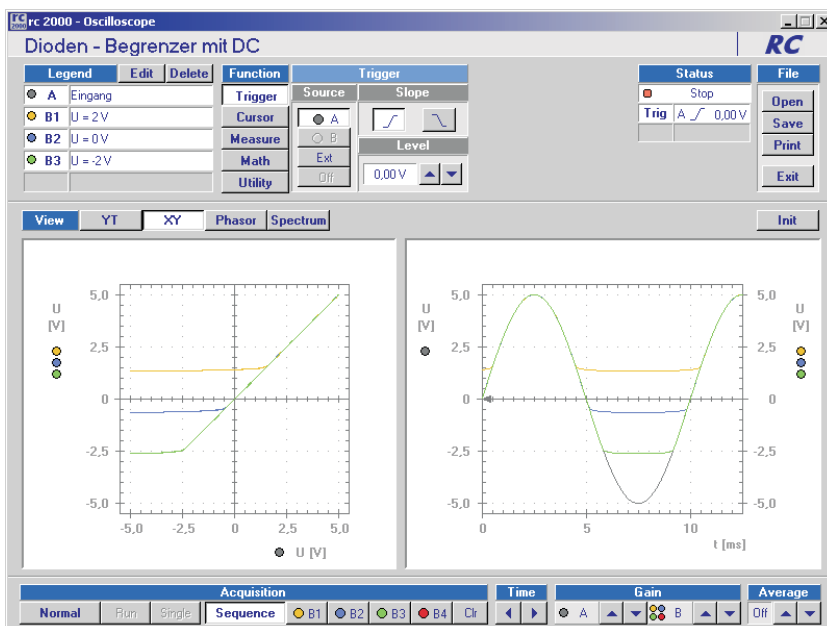

Diode limiter with DC:

- U = 2 V
- U = 0 V
- U = -2 V



# Comparator with Hysteresis



## Exercise

Display the input and output voltage curves of the comparator with hysteresis.


Circuit 1 - Zero level detector

Circuit 2 - Reference level comparator

## Schematics

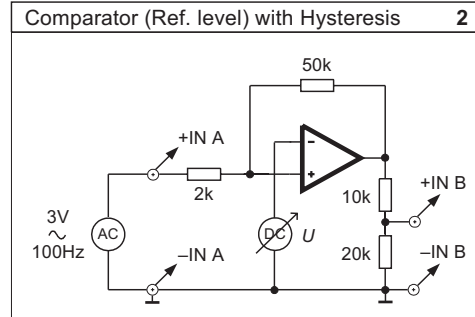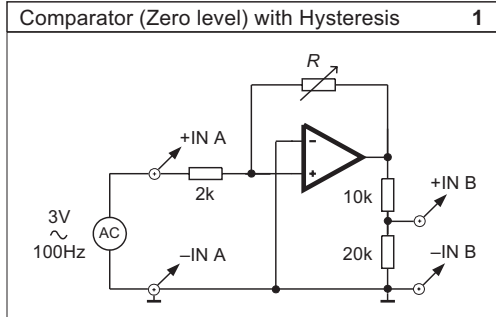


## Result

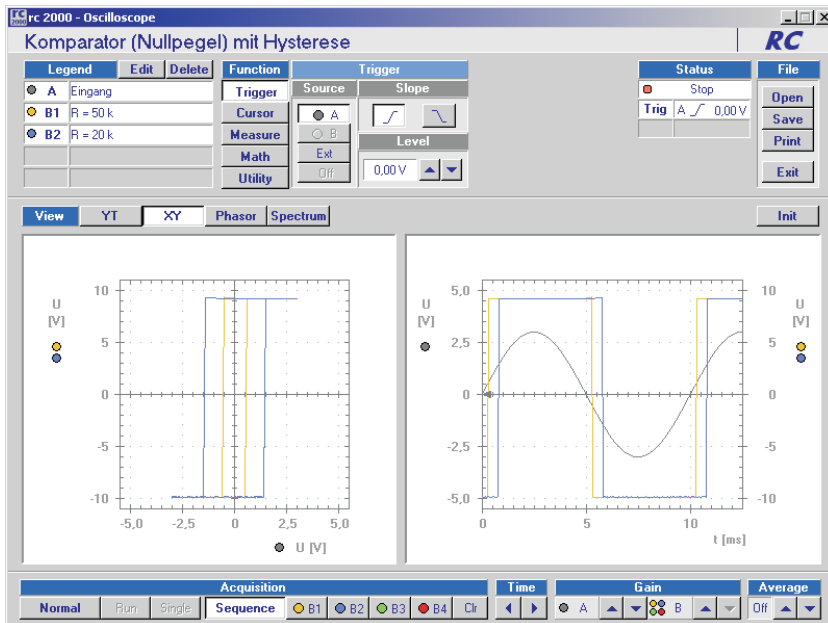

Variable hysteresis:

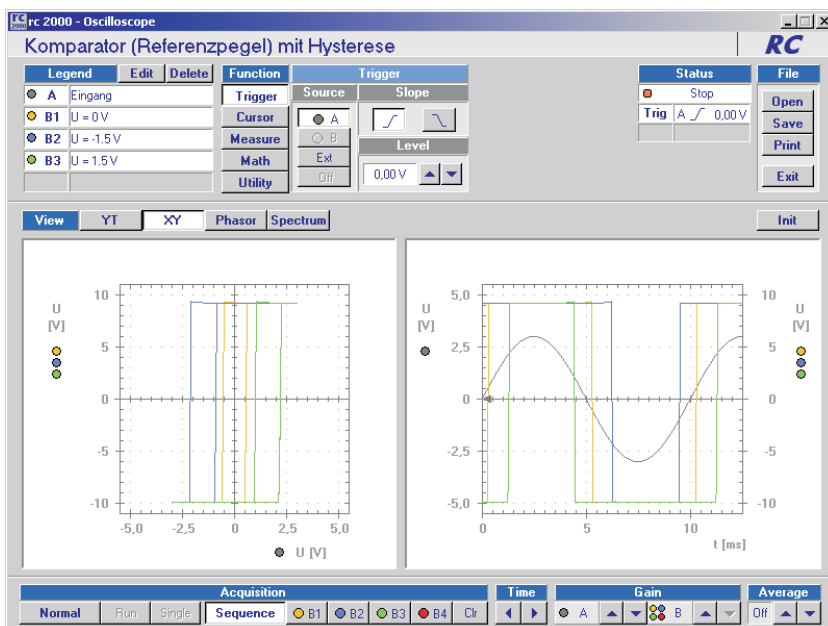- $R = 50 \text{ k}\Omega$
- $R = 20 \text{ k}\Omega$



Variable reference voltage:

- $U = 0 \text{ V}$
- $U = -1.5 \text{ V}$
- $U = 1.5 \text{ V}$


# Differential Amplifier

## Exercise

Display the  $U_1$ ,  $U_2$  and  $U_3$  voltage curves.

Using the cursor prove the validity of the equation:

## Schematics

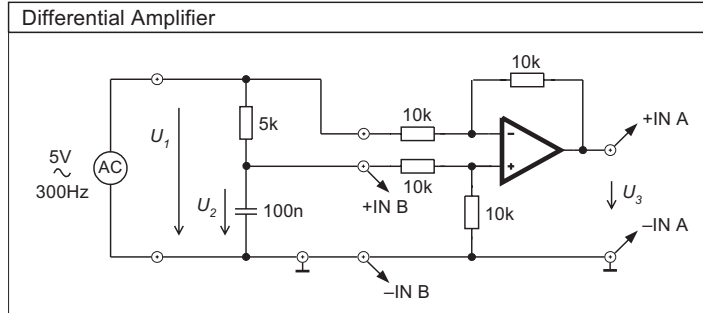


Equation:

$$U_3 = -(U_1 - U_2)$$

$$U_2 = U_3 + U_1$$

## Result

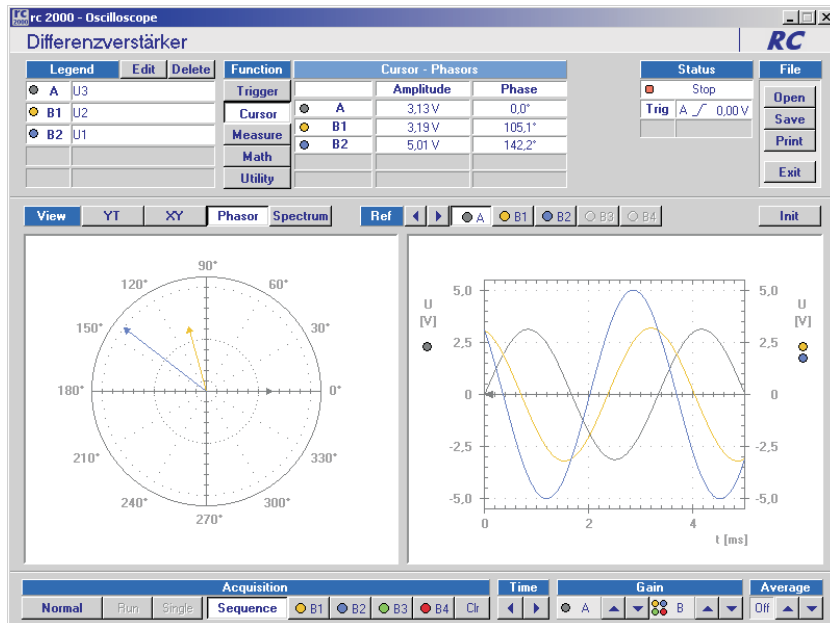

Differential amplifier:


- Output voltage  $U_3$
- Input voltage  $U_2$
- Input voltage  $U_1$

# Astable Multivibrator

## Exercise

Display the output voltage and voltage across the capacitor C.  
The output frequency is given by the equation:

## Schematics

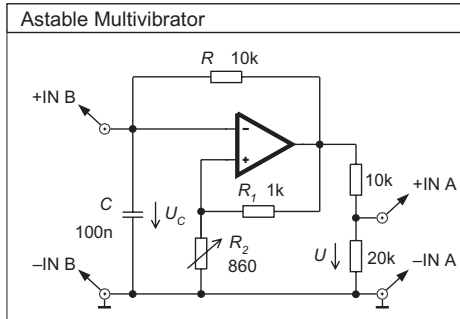


Equation:

$$R_2 = 0,86 \cdot R_1$$

$$f \cong \frac{1}{2RC}$$

## Result

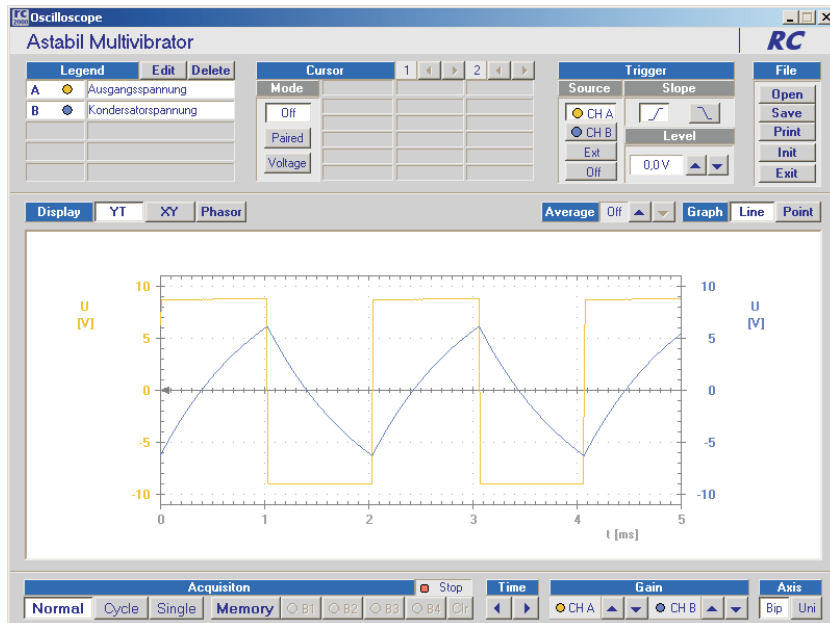

**Astable multivibrator:**

- Output voltage
- Capacitor voltage



$$f \cong 500 \text{ Hz}$$

# Phase - Shift Circuits


## Exercise

Display the amplitude and phase frequency characteristics for both circuits (all-pass filters).

## Schematics

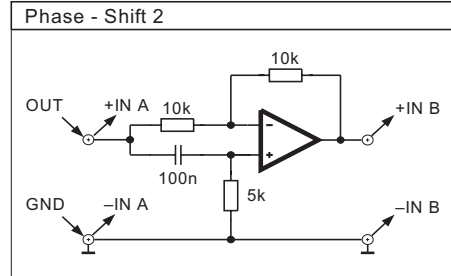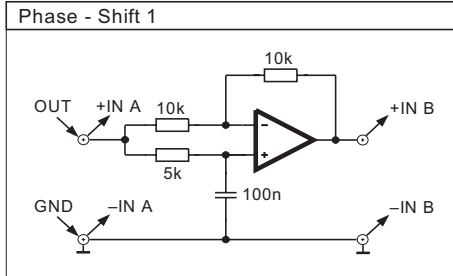


## Result

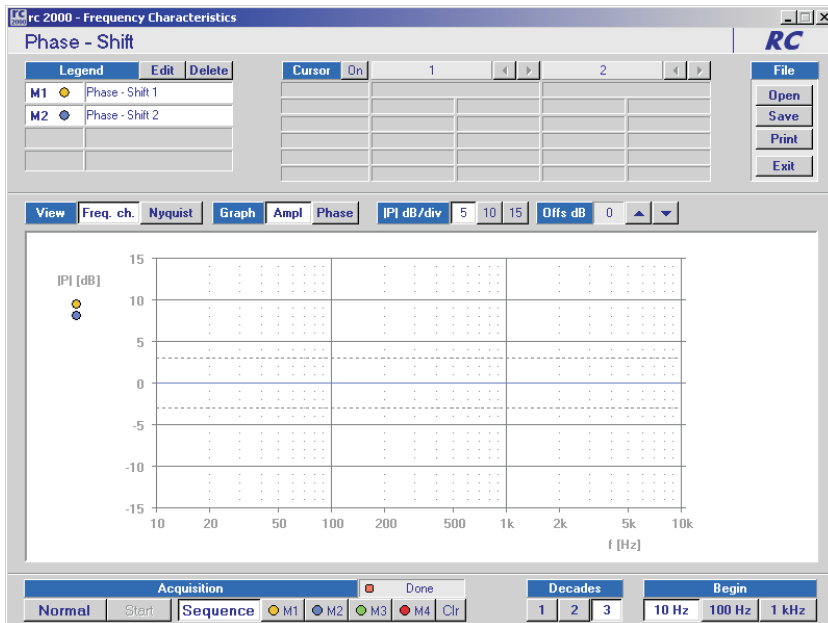

### Amplitude characteristics:

- Phase-Shift 1
- Phase-Shift 2

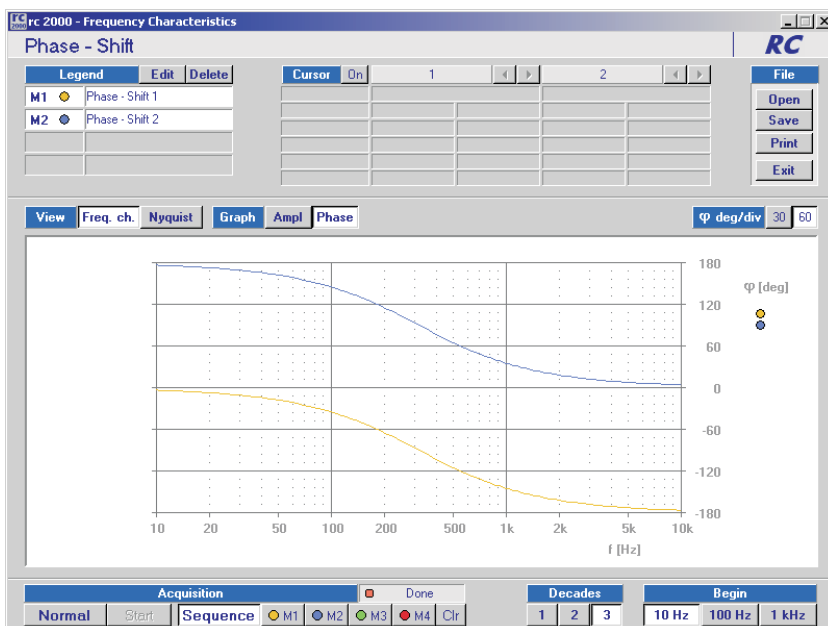

### Phase characteristics:



- Phase-Shift 1
- Phase-Shift 2

# Half-Wave Rectifier


## Exercise

Display the input and output voltage of the half-wave rectifier (schematics 1).  
Using schematics 2 display the input and output voltage of the rectifier with a capacitor filter.

## Schematics

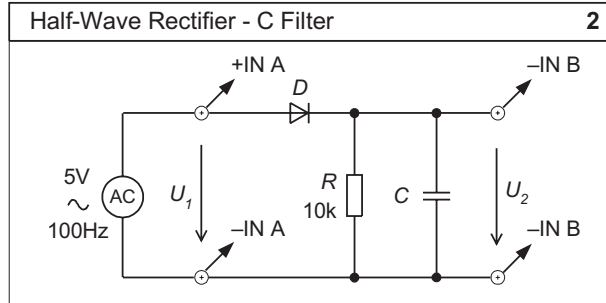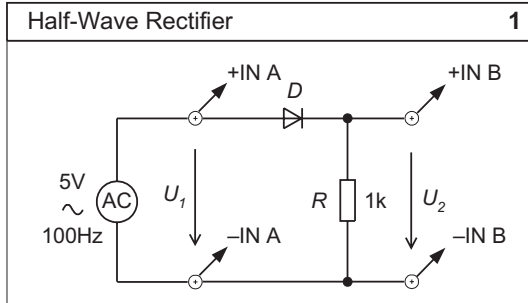


## Result

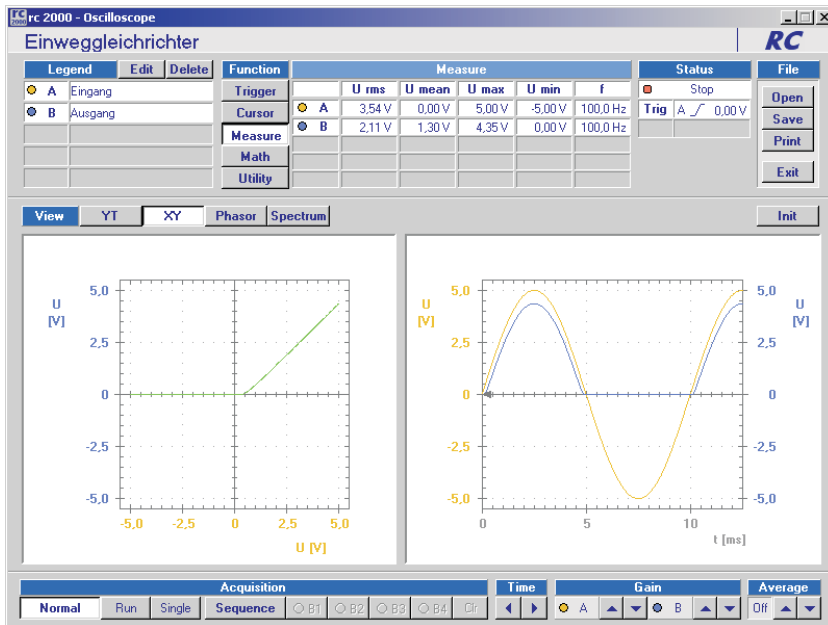

### Half-wave rectifier:

- Input
- Output

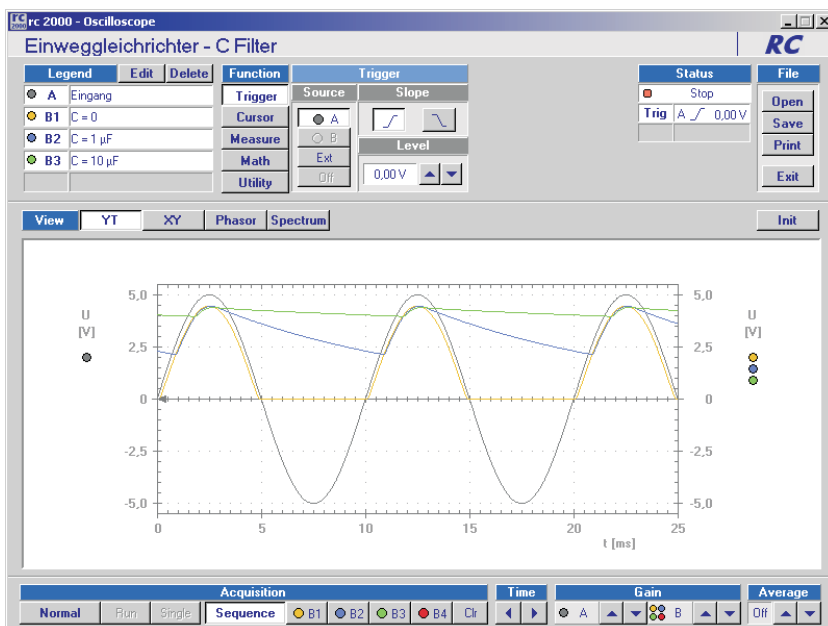

### Filter:


- C = 0
- C = 1 µF
- C = 10 µF

# Full-Wave Rectifier


## Exercise

Display the input and output voltage curve of the full-wave rectifier.

## Schematics

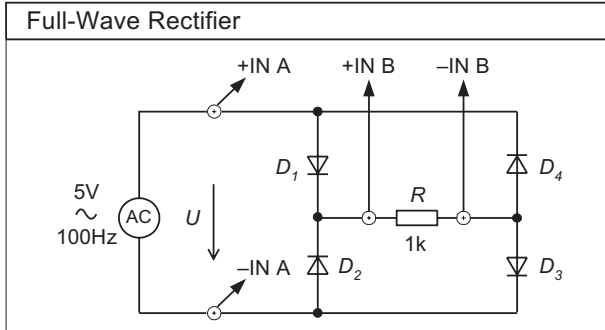


## Result

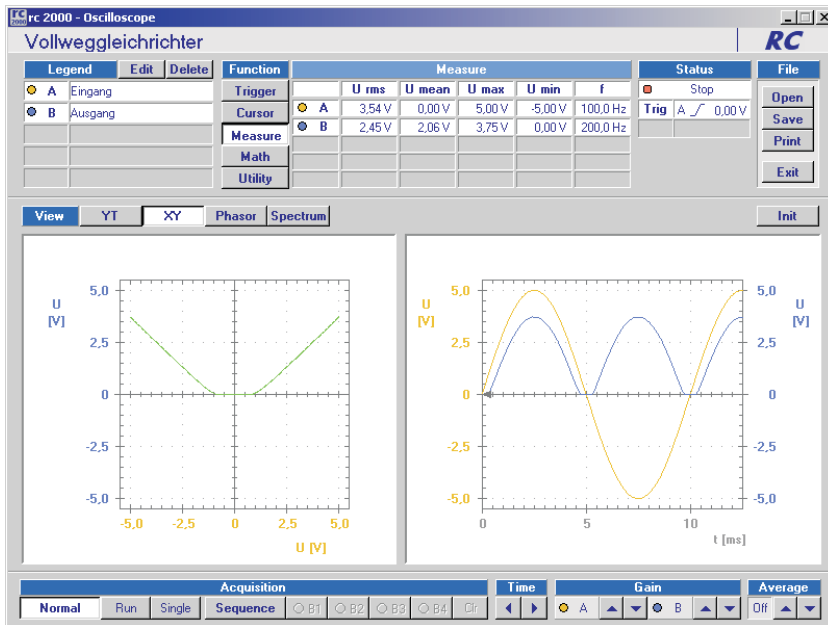

### XY Diagram:

- Input
- Output

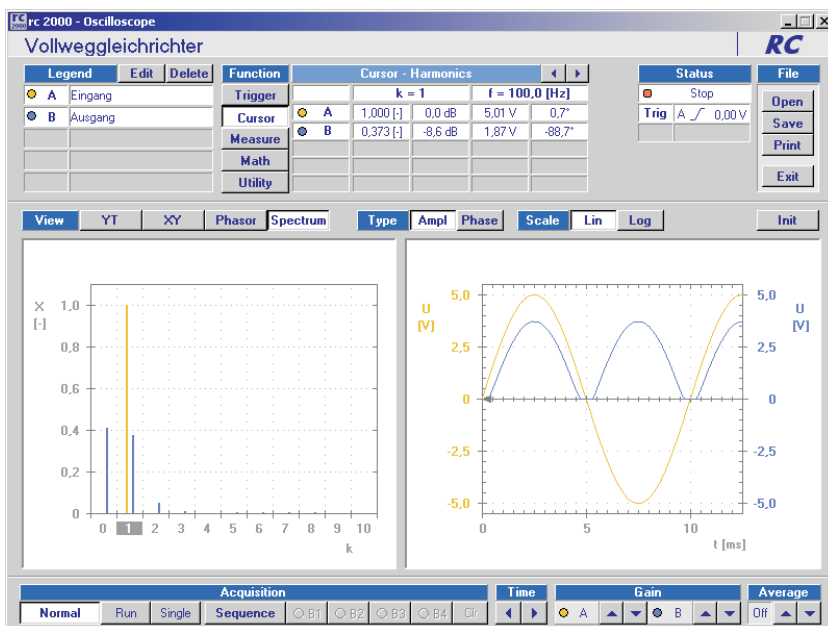

### Spectrum (Harmonics):


- Input
- Output

# Half-Wave Precision Rectifier


## Exercise

Display the input and output voltage of the OPAMP precision half-wave rectifier.

## Schematics

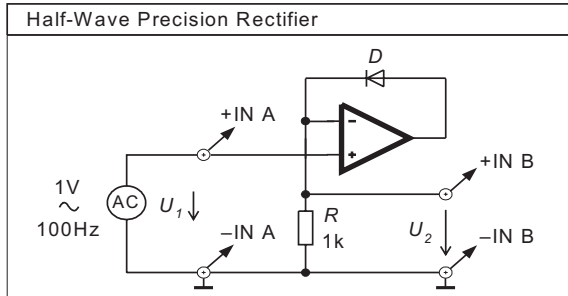

## Result

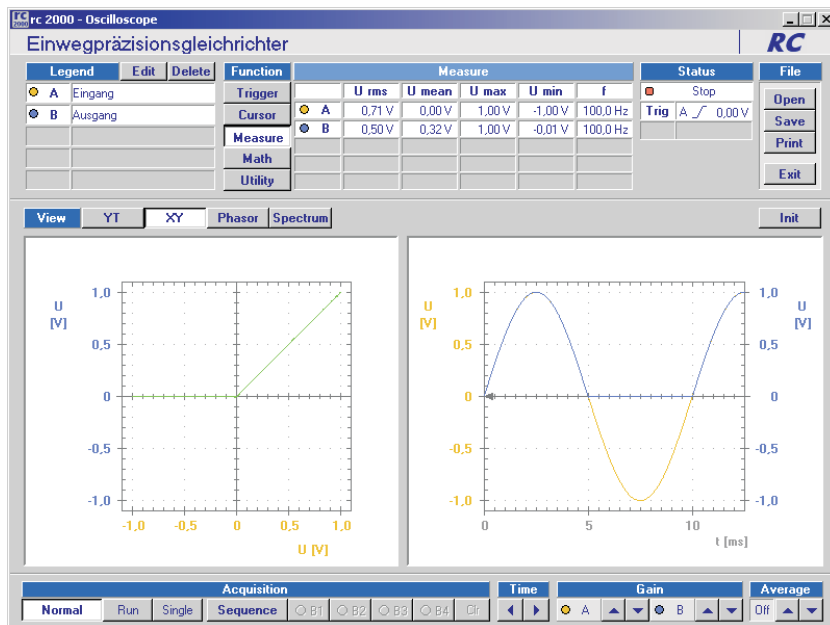

## Half-wave precision rectifier

- Input
- Output





